
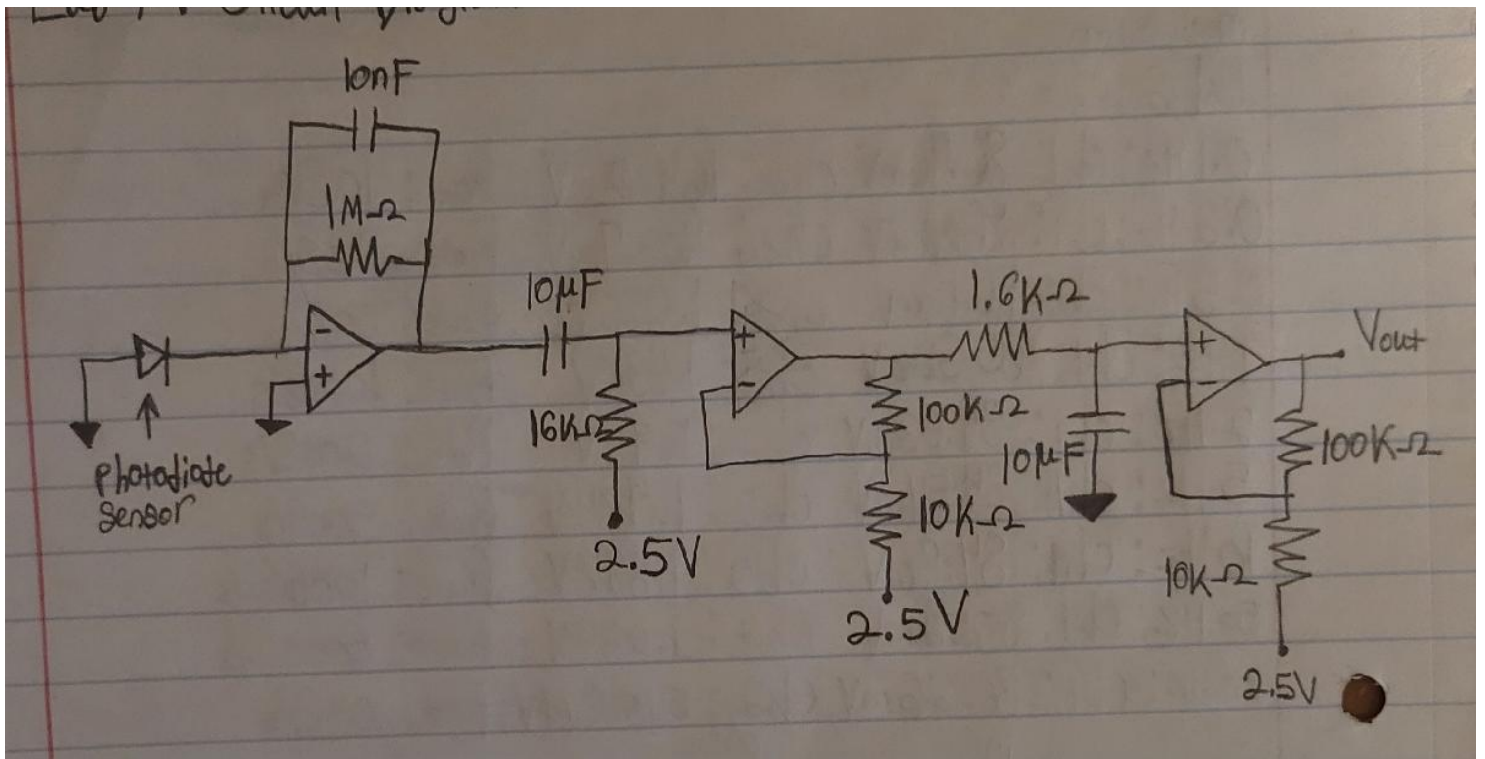


Lab 7

Final Circuit Schematic and Photo

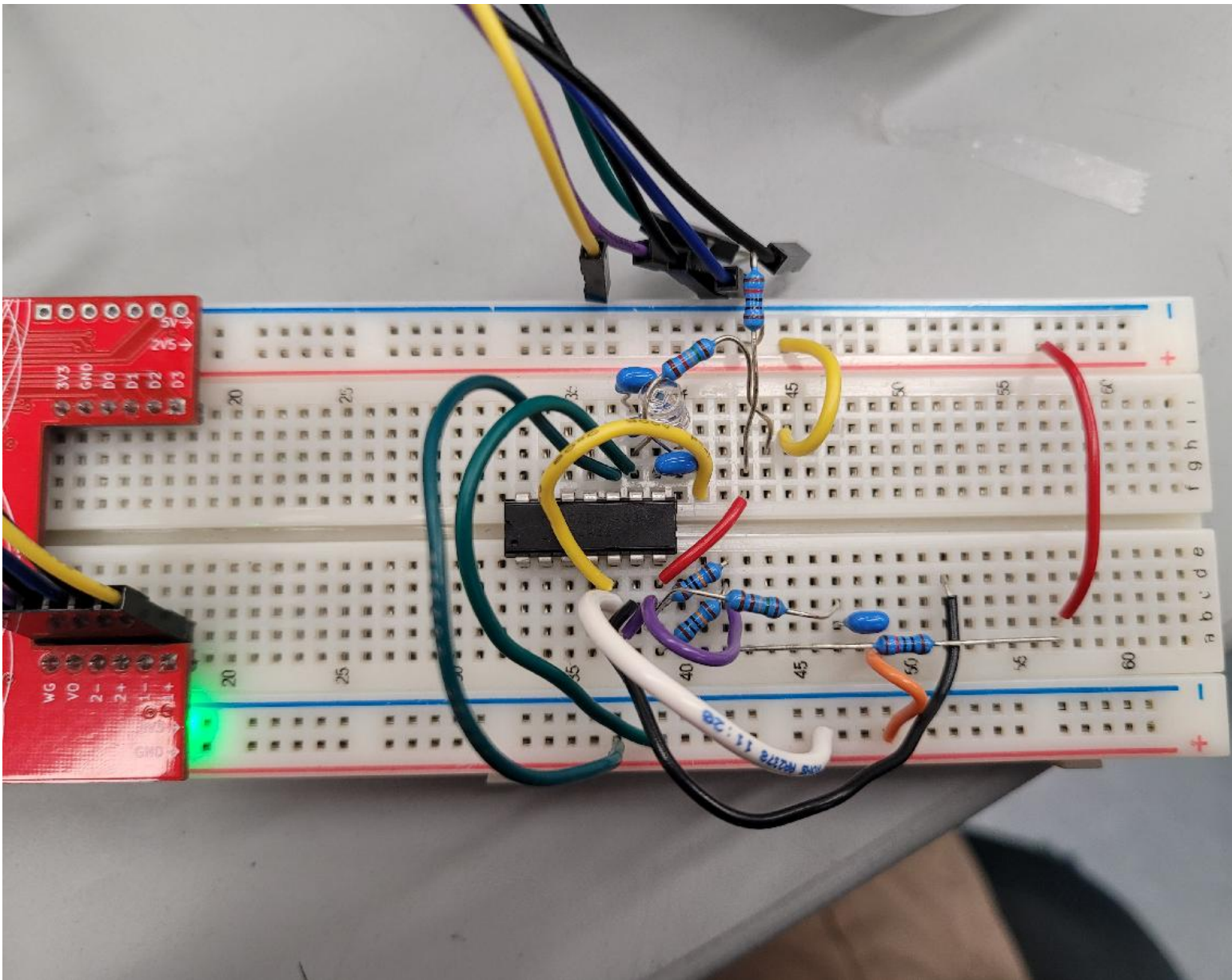




Selecting Resistor and Capacitor Values


To determine the resistor and capacitor values, I applied the formula for the cutoff frequency of a filter, $f = 1/(2\pi RC)$, to establish the desired cutoff frequencies of 1 Hz and 10 Hz. For a cutoff frequency of 1 Hz, I selected a capacitor value of 10 μF , resulting in a resistor value of approximately 158 k Ω . For a cutoff frequency of 10 Hz, I chose a capacitor value of 1 μF , yielding a resistor value of around 1.58 k Ω . Additionally, to achieve an amplifier gain of approximately 10, I used the gain equation, $\text{Gain} = (R1 + R2)/R2$, where $R1 \gg R2$. With this, I determined resistor values of 100 k Ω for $R1$ and 10 k Ω for $R2$.

Bode Plot

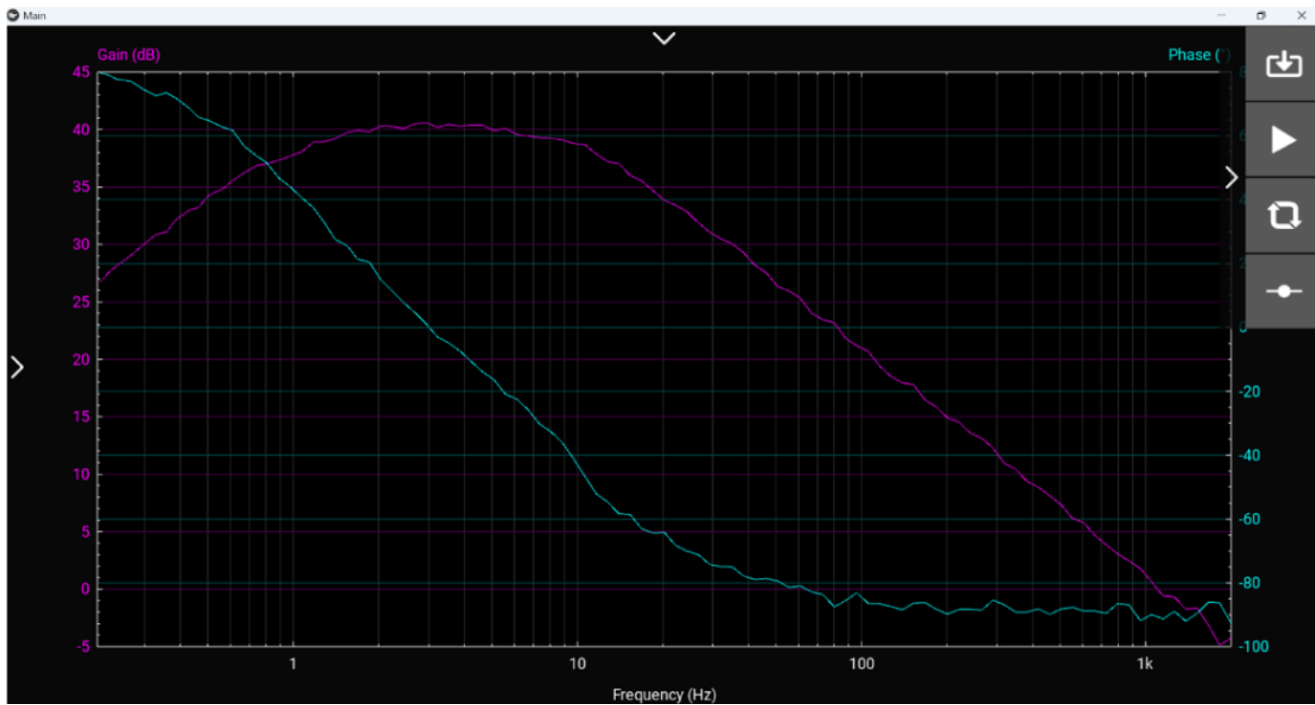

The bode plot (Gain (dB) vs. Frequency (Hz)) for the pulse oximeter to observe the cut-off frequencies of the circuit.

Scope Trace of Pulse

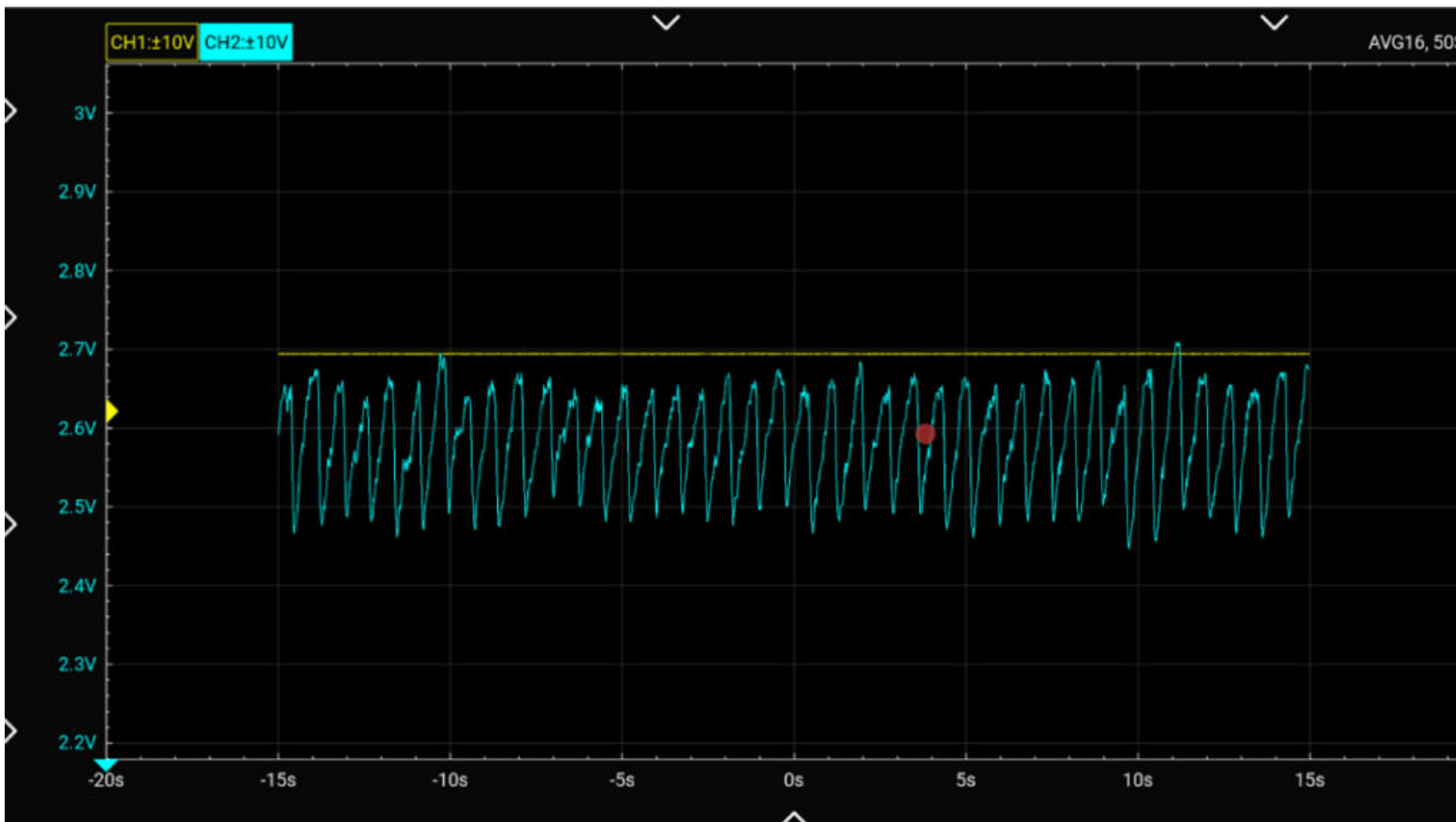

A scope trace of a pulse using the pulse oximeter circuit.